

## The Wiring Diagram

### Wiring Instructions

Follow these instructions to ensure that your Arduinos will run properly.  
Please wire the Arduinos together before connecting them to the computer.

#### LED Screen to Arduino(For both Arduinos):

1. GND <---> Breadboard GND bus
2. VCC <---> Breadboard Positive bus
3. RESET <--> Pin 8
4. D/C <---> Pin 7
5. CARD\_CS <---> Pin 5
6. TFT\_CS <---> Pin 6
7. MOSI <---> Pin 51
8. SCK <---> Pin 52
9. MISO <---> Pin 50
10. LITE <---> Breadboard Positive bus

#### Joystick to Arduino(For both Arduinos):

1. VCC <---> Breadboard Positive bus
2. VERT <---> Pin A0
3. HOR <---> Pin A1
4. SEL <---> Pin 9
5. GND <---> Breadboard GND bus

#### Pushbutton to Arduino(For both Arduinos):

1. Pin 2 <---> Pushbutton <---> Breadboard GND bus

#### Arduino to Arduino:

1. Arduino 1 GND <---> Arduino 2 GND
2. Arduino 1 TX3 <---> Arduino 2 RX3
3. Arduino 1 RX3 <---> Arduino 2 TX3

#### Other Wiring:

##### Server Arduino:

1. Pin 13 <---> Resistor <---> Breadboard GND bus


##### Client Arduino:

1. Pin 13 <---> Arduino GND


##### Both Arduinos:

1. Arduino 5V <---> Breadboard Positive bus
2. Arduino GND <---> Breadboard GND bus

The wiring diagram for the server:

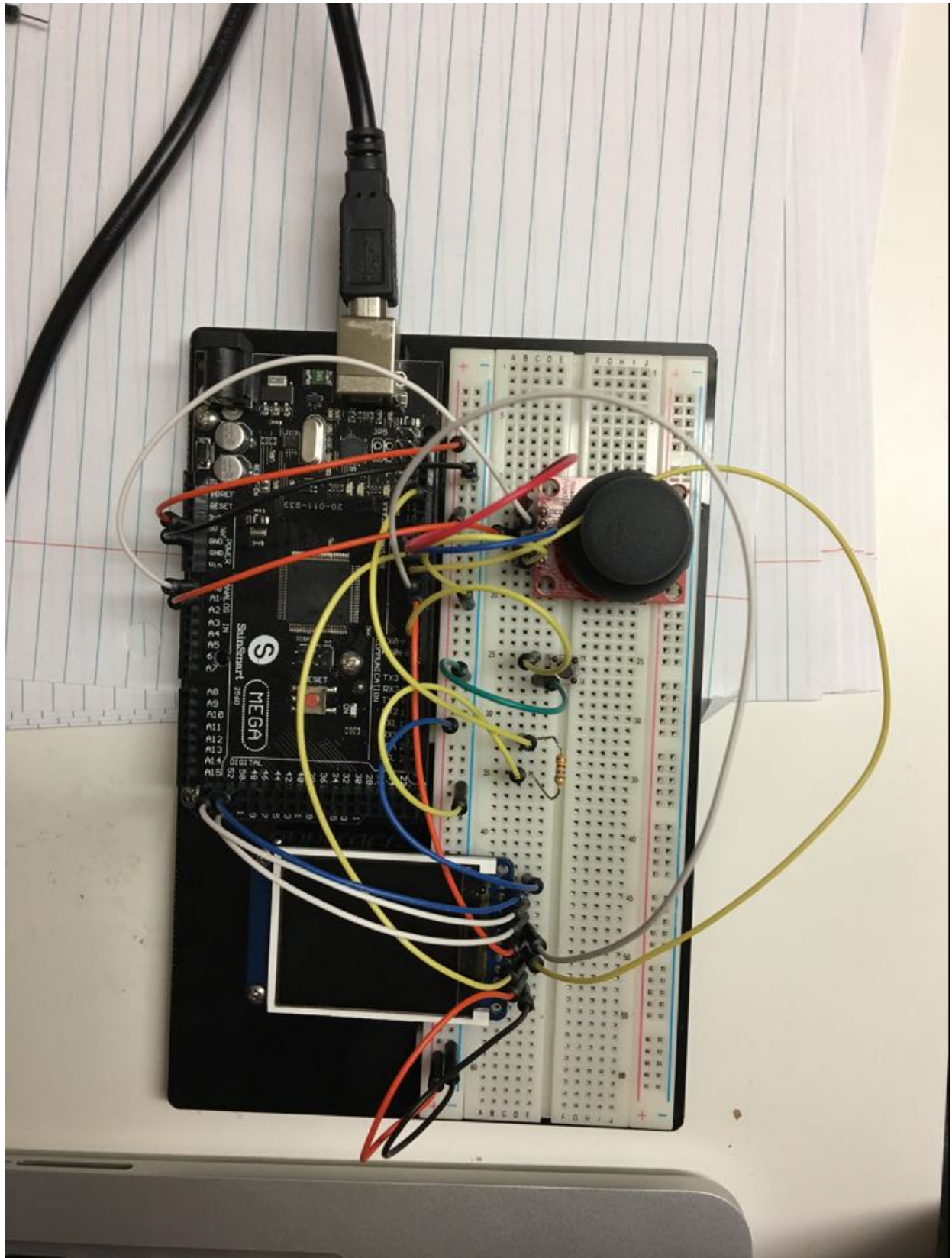

The wiring diagram for the client:

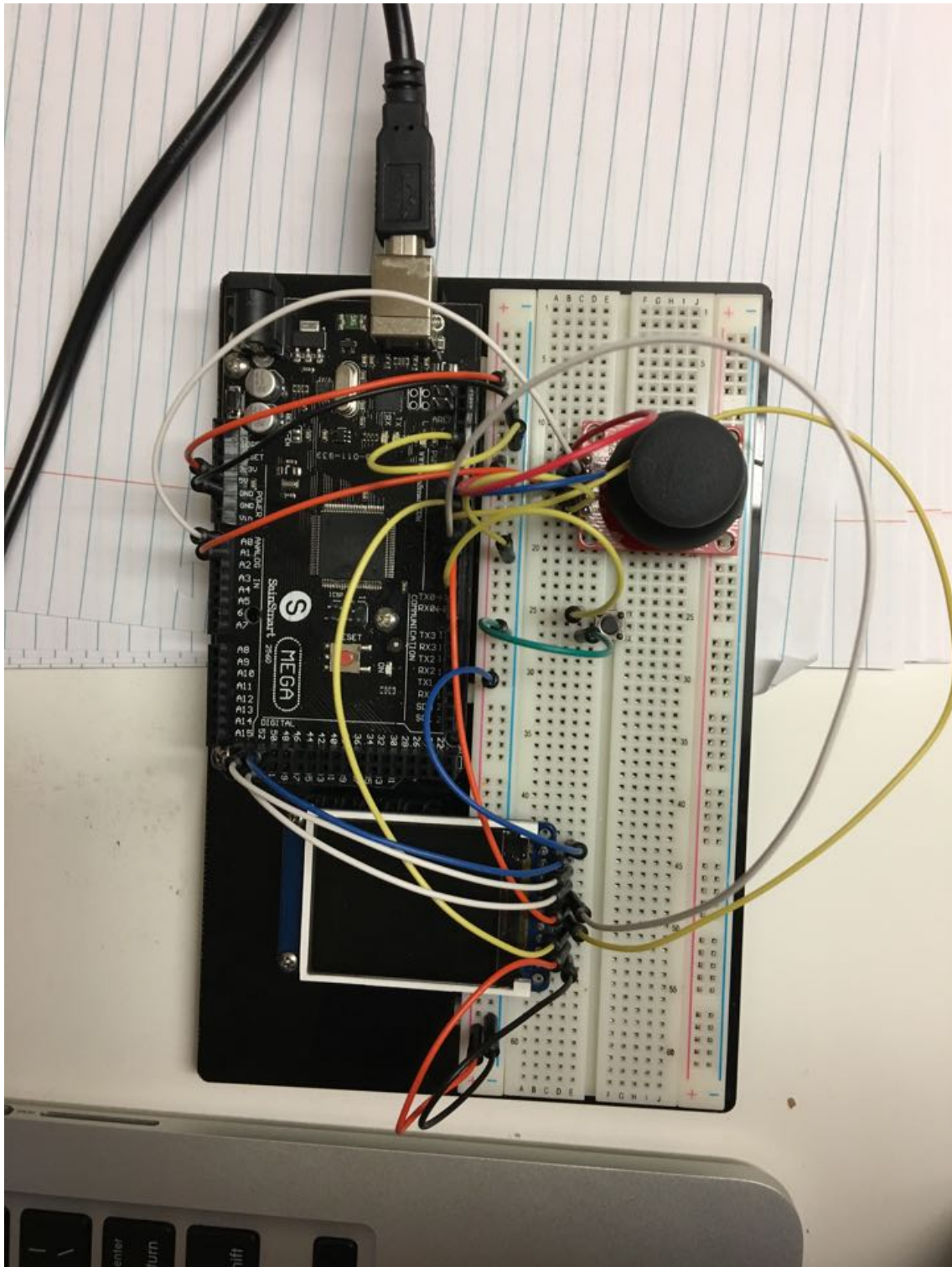

To connect these two Arduino together, please connect Arduino 1 GND to Arduino 2 GND, Arduino 1 TX3 to Arduino 2 RX3, and Arduino 1 RX3 to Arduino 2 TX3.